

Computationally Asymmetric Permutations and Reversible-gates Circuits

One Approach to One-Wayness

Alexey E. Zhukov

Bauman Moscow Technical University

E-mail: aez_iu8@rambler.ru

Permutations on \mathbb{Z}_2^n



$(x_2 x_1 x_0)$	$(y_2 y_1 y_0)$
0 0 0	0 1 1
0 0 1	1 0 0
0 1 0	1 0 1
0 1 1	0 0 1
1 0 0	1 1 1
1 0 1	0 1 0
1 1 0	0 0 0
1 1 1	1 1 0

$$\mathbf{F} : \mathbb{Z}_2^3 \rightarrow \mathbb{Z}_2^3$$


$(y_2 y_1 y_0)$	$(x_2 x_1 x_0)$
0 0 0	1 1 0
0 0 1	0 1 1
0 1 0	1 0 1
0 1 1	0 0 0
1 0 0	0 0 1
1 0 1	0 1 0
1 1 0	1 1 1
1 1 1	1 0 0

$$\mathbf{F}^{-1} : \mathbb{Z}_2^3 \rightarrow \mathbb{Z}_2^3$$


Logical Gate Circuits

$(x_2 x_1 x_0)$	$(y_2 y_1 y_0)$
0 0 0	0 1 1
0 0 1	1 0 0
0 1 0	1 0 1
0 1 1	0 0 1
1 0 0	1 1 1
1 0 1	0 1 0
1 1 0	0 0 0
1 1 1	1 1 0


$$L(F) = 7$$

 

Computationally Asymmetric Permutations

 


$$L(F)=7$$

 

$$L(F^{-1})=8$$

Computationally Asymmetric Linear Permutations



Boppana R.B., Lagarias J.C. *One-way functions and circuit complexity*. Information and Computation, vol. 74 (1987), pp. 226-240

Hiltgen A.P. *Constructions of feebly-one-way families of permutations*. AUSCRYPT'92, LNCS v.718 (1993), pp. 422-434



Computationally Asymmetric Linear Permutations

$$\mathbf{A} : \mathbb{Z}_2^n \rightarrow \mathbb{Z}_2^n$$

$$y_i(x_1, \dots, x_n) = x_i \oplus x_{i+1}, \quad i = 1, \dots, n-1;$$

$$y_n(x_1, \dots, x_n) = x_1 \oplus x_{\lceil n/2 \rceil} \oplus x_n$$

$$L(\mathbf{A}) = n + 1 \qquad L(\mathbf{A}^{-1}) = \frac{3(n-1)}{2}$$

for $n = 7$:

$$L(\mathbf{A}) = 8 \qquad L(\mathbf{A}^{-1}) = 9$$

Computationally Asymmetric Linear Permutations

for $n = 7$:

$$\mathbf{A} = \begin{pmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 & 1 \end{pmatrix}$$

$$\mathbf{A}^{-1} = \begin{pmatrix} 0 & 0 & 0 & 1 & 1 & 1 & 1 \\ 1 & 0 & 0 & 1 & 1 & 1 & 1 \\ 1 & 1 & 0 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 0 & 1 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 0 & 0 & 0 & 1 \end{pmatrix}$$

$$L(\mathbf{A}) = n + 1 \underset{(n=7)}{=} 8$$

$$L(\mathbf{A}^{-1}) = \frac{3}{2}(n - 1) \underset{(n=7)}{=} 9$$



Reversible Gates

NOT



$$x \text{ --- } \otimes \text{ --- } \bar{x} = x \oplus 1$$

$$\bar{x} \text{ --- } \otimes \text{ --- } x$$

CNOT (Controlled NOT)

  

  Toffoli's CCNOT (Controlled Controlled NOT)






$$\mathbf{A} = \begin{pmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 & 1 \end{pmatrix}$$

Reversible-gates Circuit

for odd $n \geq 7$:
 
$$L(\mathbf{A}) = n + 1 = 8 \quad (n=7)$$






$$\mathbf{A} = \begin{pmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 1 \\ 1 & 0 & 0 & 1 & 0 & 0 & 1 \end{pmatrix}$$


Reversible-gates Circuit

for odd $n \geq 7$:

 
$$L(\mathbf{A}) = n + 1 = 8 \quad (n=7)$$



Reversible Circuit

 


Reversible Circuit

 



for odd $n \geq 7$:

 
$$L(\mathbf{A}) = n + 1 \underset{(n=7)}{=} 8$$





for odd $n \geq 7$:

 
$$L(\mathbf{A}^{-1}) = \frac{3}{2}(n-1) \underset{(n=7)}{=} 9$$






for odd $n \geq 7$:
 
$$L(\mathbf{A}^{-1}) = n \underset{(n=7)}{=} 7$$




Reversible-gates Circuit for Two-number Adder

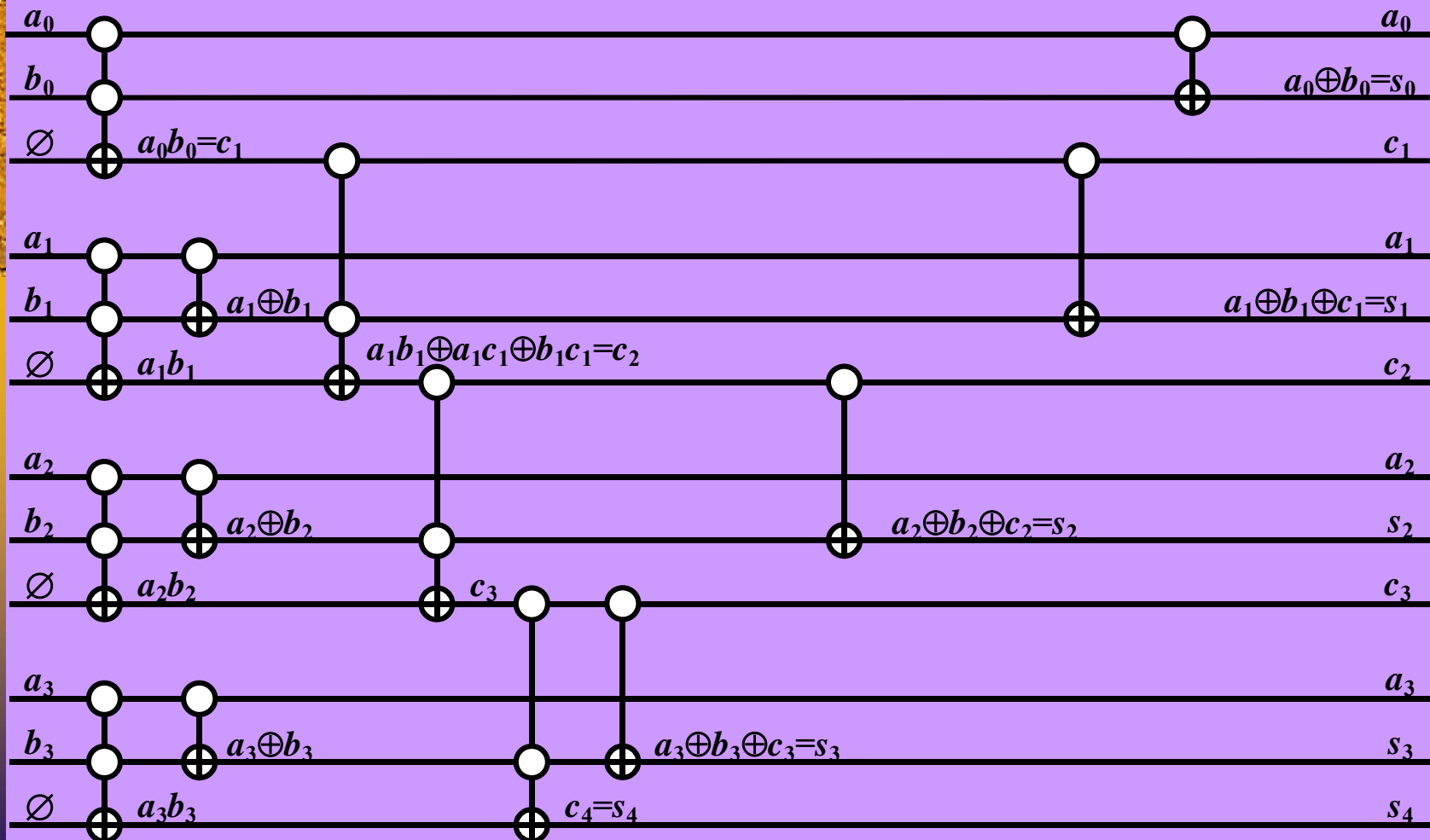
$L = 5n - 3$: Red'kin N.L. *Minimal realization of a binary adder*. Probl. Kibern., 38 (1981), pp. 181-216



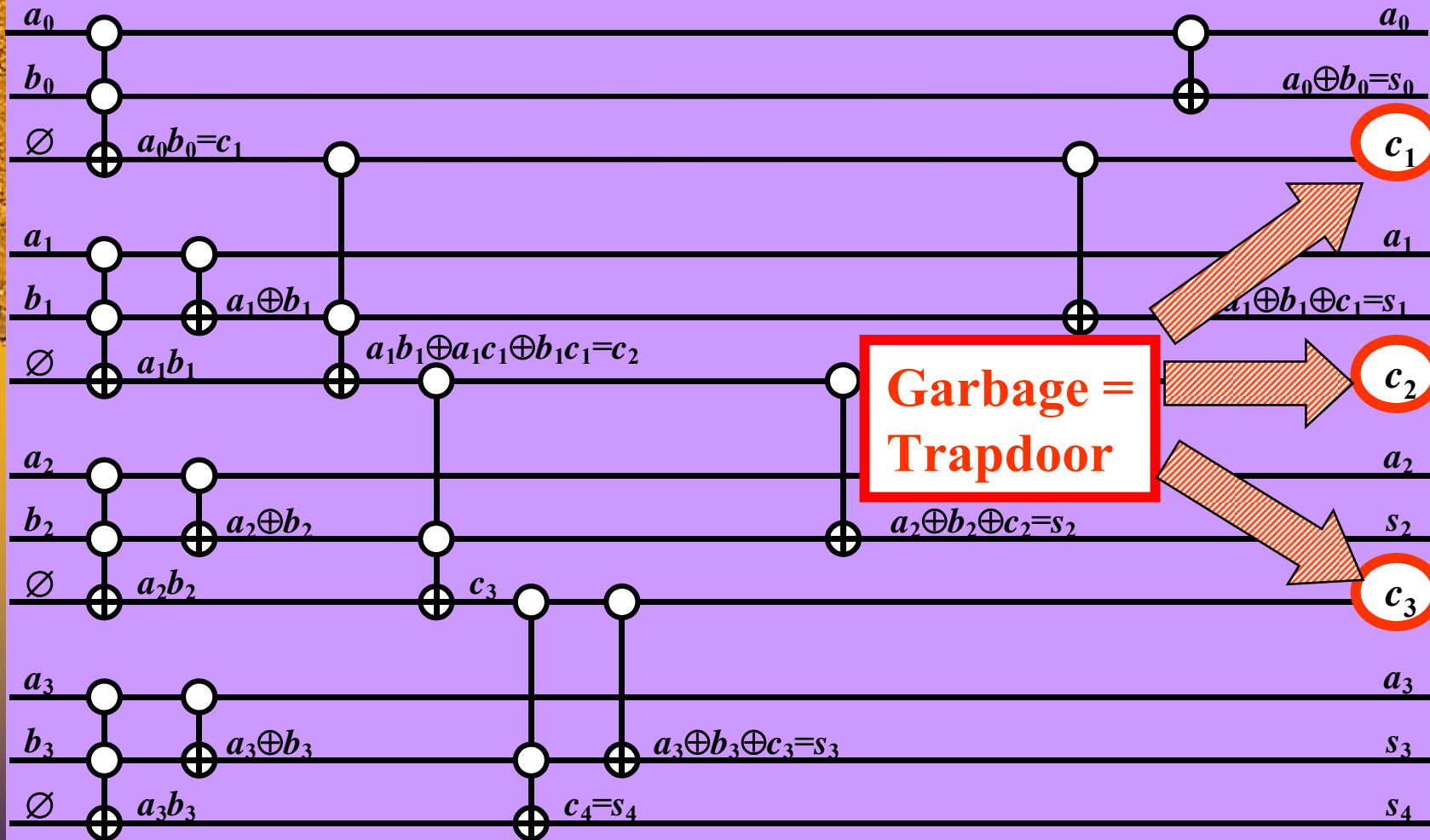
Reversible-gates Circuit for Two-number Adder



Reversible Circuit for Two-number Adder

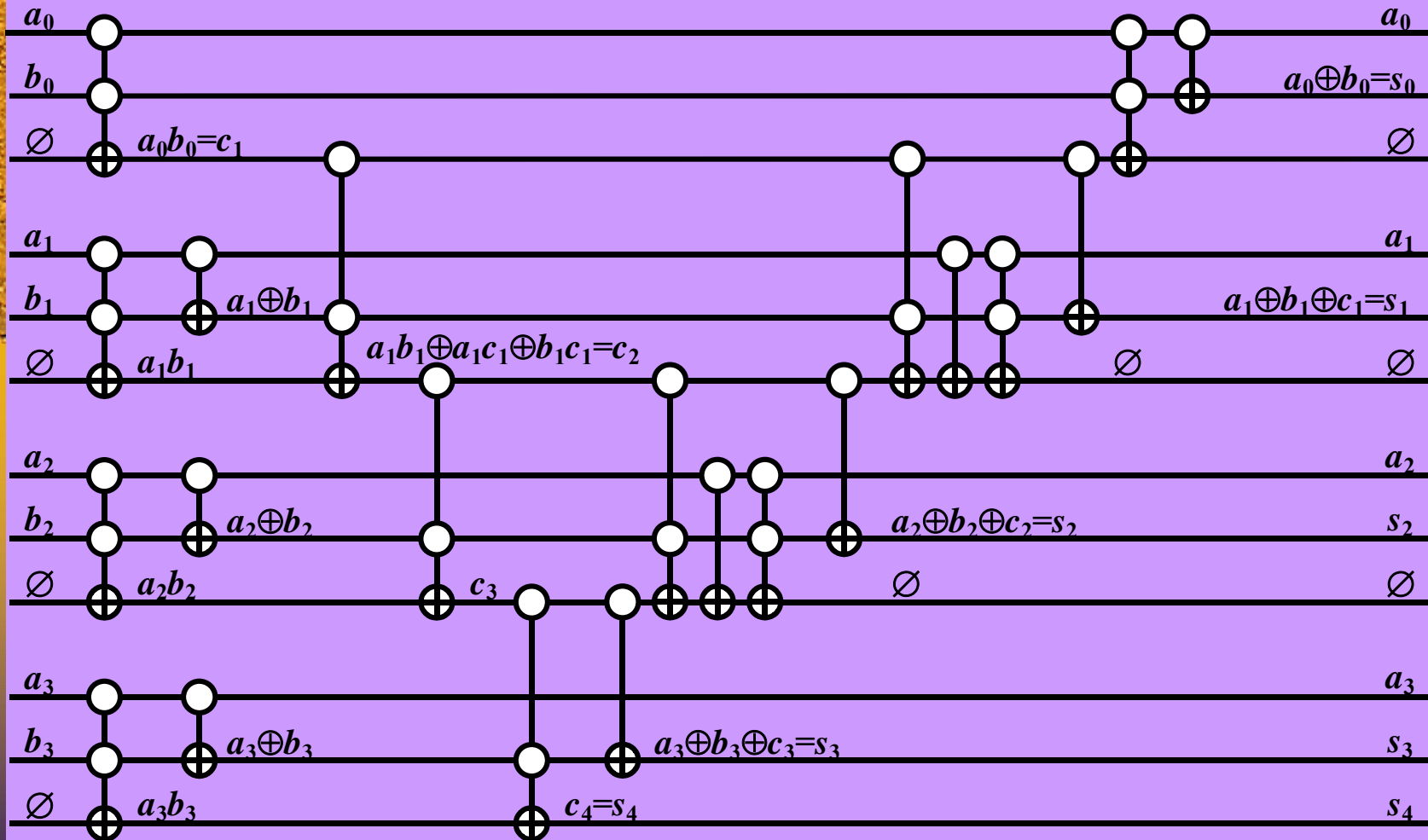

Reversible Circuit for Two-number Adder

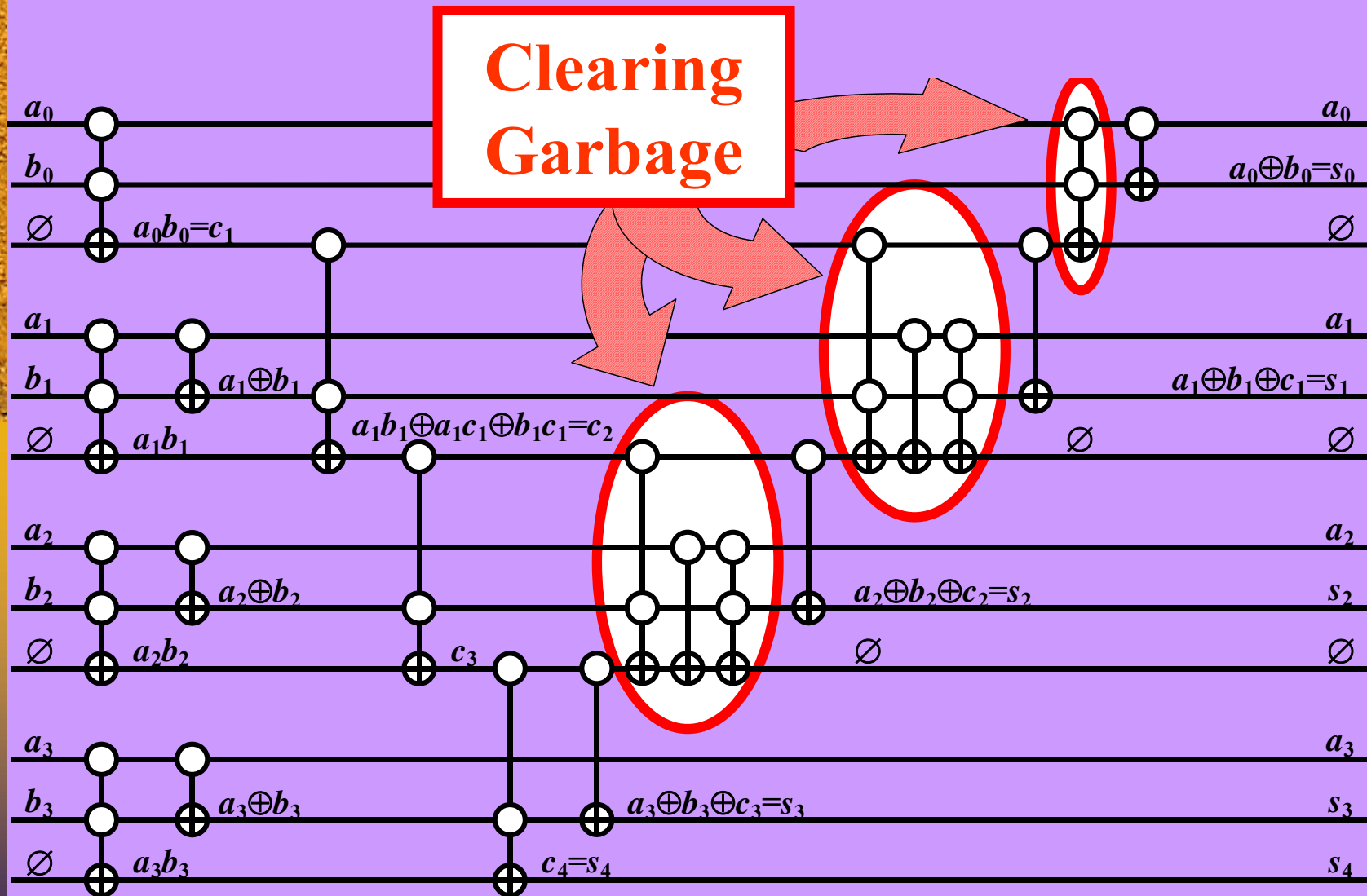

Reversible Circuit for Two-number Adder

